

Basic Electronics Engineering


Bias: Application of external voltage across the two terminal

i) No bias: Diffusion Current: Due to majority Charge carrier


Drift Current: Due to minority Charge carrier

Net Current = 0


ii) Forward Bias:

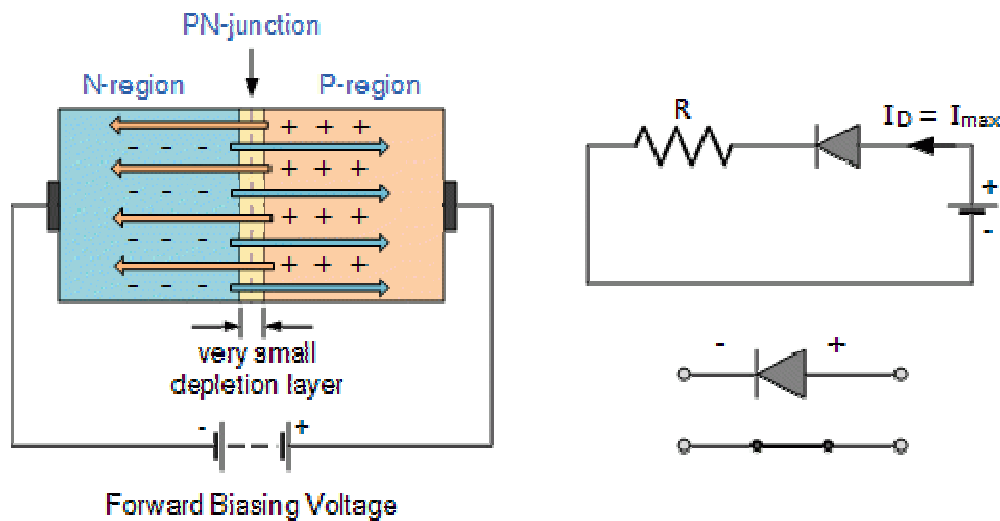


iii) Reverse Bias:

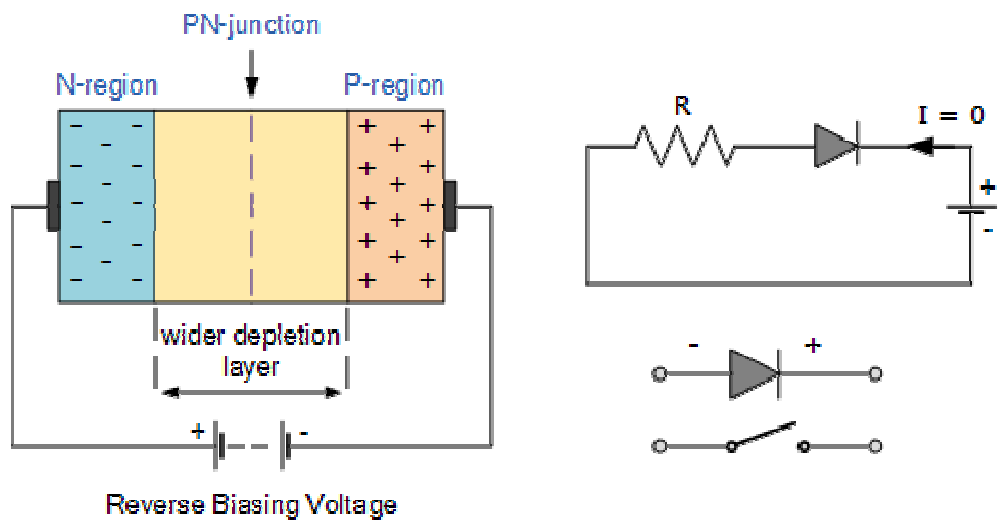

V-I characteristics of a diode:

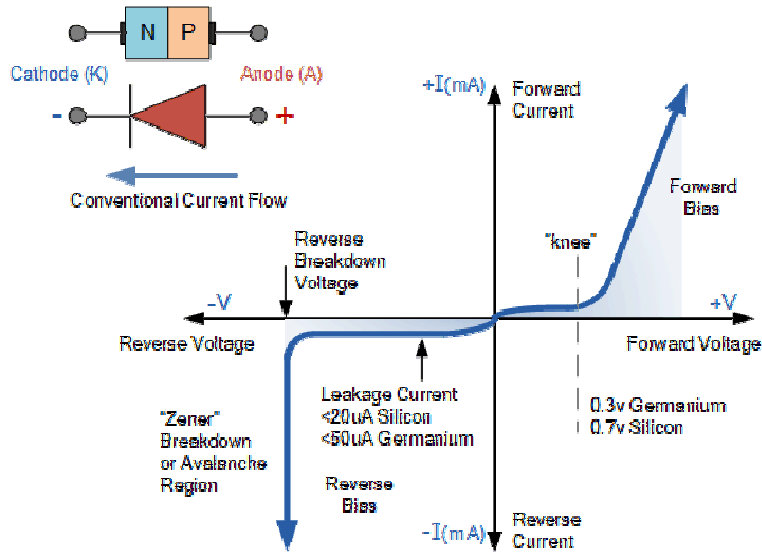

Load line analysis:

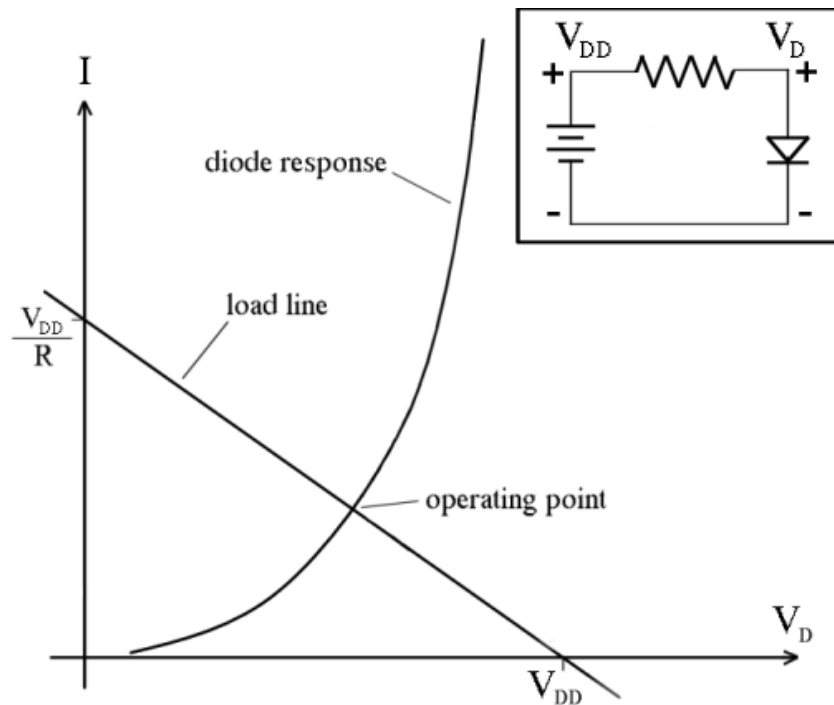

$$+E - V_D - V_R = 0$$

$$E = V_D + I_D R$$

$$I_D = \frac{E}{R} \Big|_{V_D=0 \text{ V}}$$

$$V_D = E \Big|_{I_D=0 \text{ A}}$$